

Reading 08


10.1 Decoders, Demuxes, and Muxes

4 way decoder

↳ 4 outputs

↳ 2 select-lines


↳ only 1 output is high (1) at a time

 

1-to-4 Demultiplexer (Demux)

↳ essentially same as decoder

↳ but the output has value d

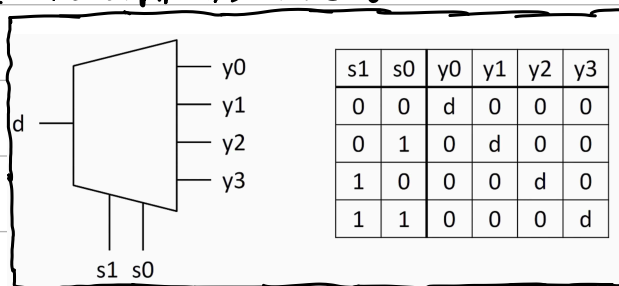


4-to-1 Multiplexer (Mux)

↳ 4 data inputs (d_0, d_1, d_2, d_3)

↳ 2 select lines (s_0, s_1)

↳ single output (y)

 


11.1 Decoders

- A decoder is a combinational circuit that converts N inputs to a 1 on one of 2^N outputs.


↳ A 2×4 decoder ("2 to 4 decoder") converts two inputs to a 1 on exactly one of 4 outputs.

• **Ex** of decoder to circuit!

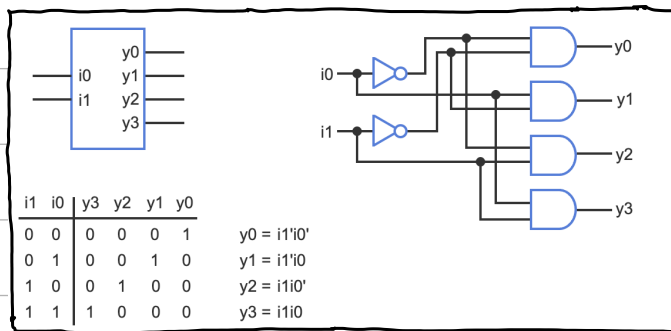

- Remember N inputs to 2^N outputs
- Remember each output requires 1 AND gate.
- Remember decoders do NOT require an OR gate.
- Some decoders have an additional input called enable input that when 0 sets all outputs to 0s, and when 1 enables the decoder's normal behavior.

↳ **Ex**

 

11.2 Muxes




• A multiplexer is a combinational circuit that passes one of multiple data inputs through to a single output, selecting which one based on additional control inputs.

↳ Mux is short for multiplexor

↳ A mux's control inputs are called select lines.

• A 4x1 mux, "4 to 1" mux has 4 data inputs, one data output, and requires two select pins.

 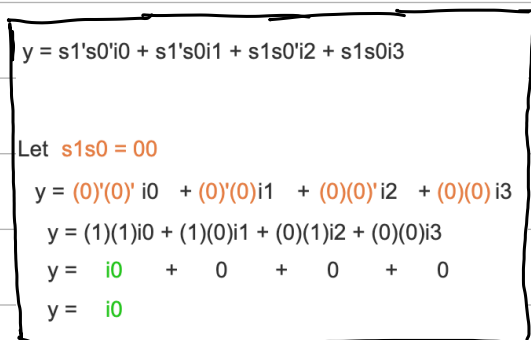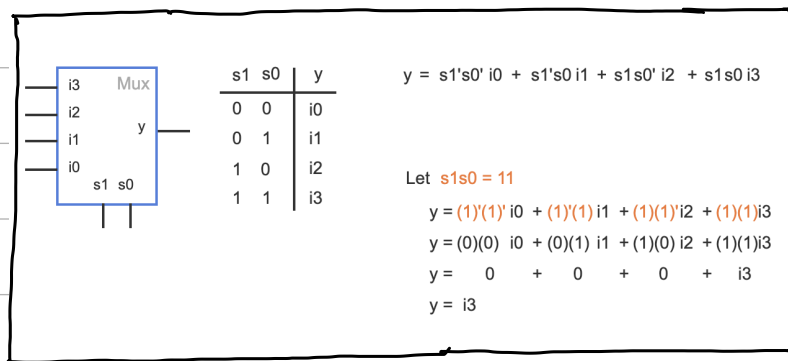
↳ Analogy: 4 lanes merge into 1 lane due to construction. A policeman (the select input) selects which one lane currently passes through by blocking the other lanes.



• For N data inputs, a mux requires $\log_2 N$ select inputs.

↳ It also requires one AND gate per input, and an individual OR gate.



11.3 N-bit muxes

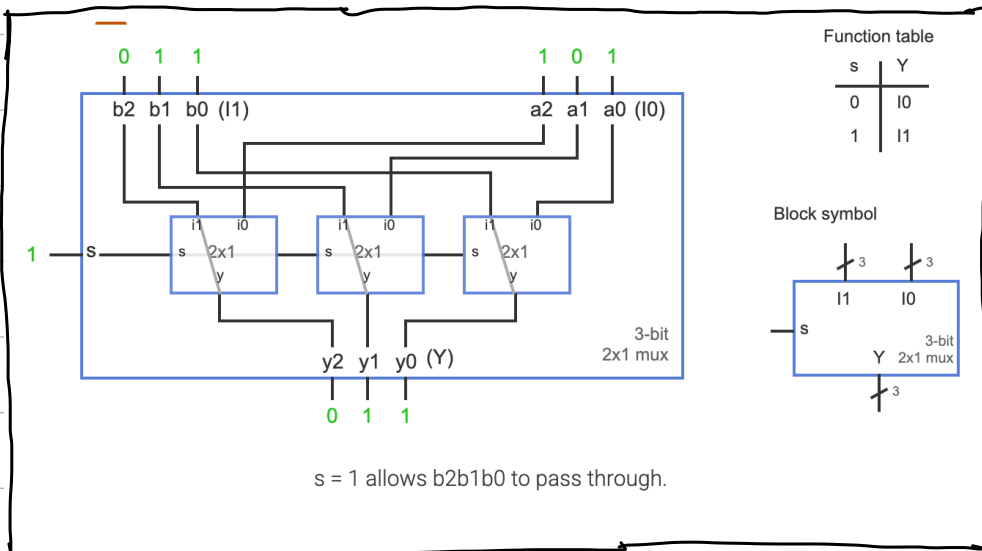


3 bit 2x1 Mux

 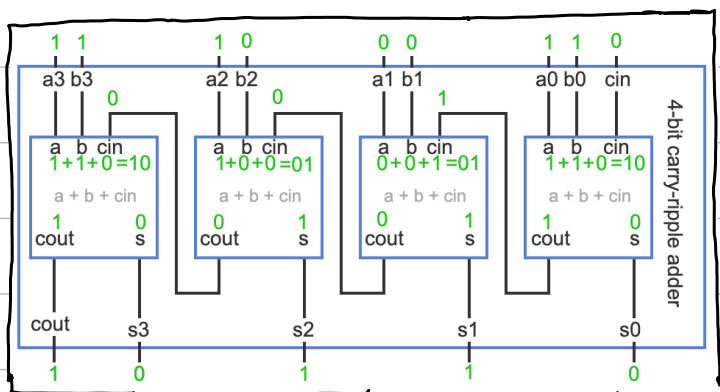11.4 Adders

- An adder computes $A+B$, where A and B are N -bit numbers, such as 8-bit numbers. A carry-ripple adder mimics adding by hand, adding a digit's pair of bits and carry-in bit, and generating a sum and carry-out bit.



Notation:

 

• Each digit's pair of bits and carry-in bit are added simultaneously.

↳ As carry bits propagate from right to left, each digit's pair and carry-in are re-evaluated.


• A half adder is a circuit that adds two bits and generates a sum and carry-out bit.

• A full adder is a circuit that adds three bits and generates a sum and carry-out.

↳ can be designed from a truth table:

ci	a	b	co	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

0	10	11
0	1	1
+0	+1	+1
00	10	11

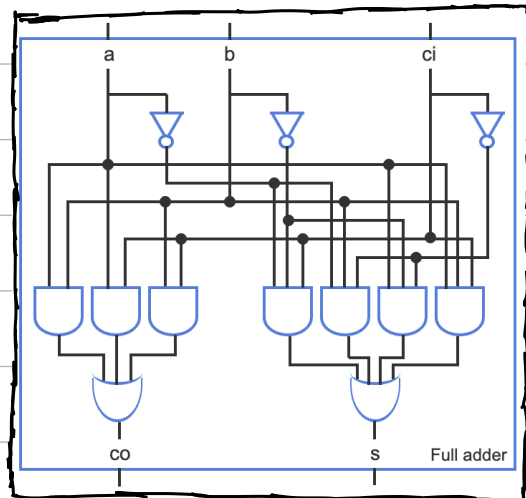

$$co = ci'ab + cia'b + ciab' + ciab$$

$$co = ab + cia + cib$$


$$s = ci'a'b + ci'ab' + cia'b' + ciab$$

• An N bit carry-ripple adder is constructed with N full adders.

• An incrementer adds 1 to a number.

• A half adder adds 2 bits (a,b) and is sufficient for an incrementer.

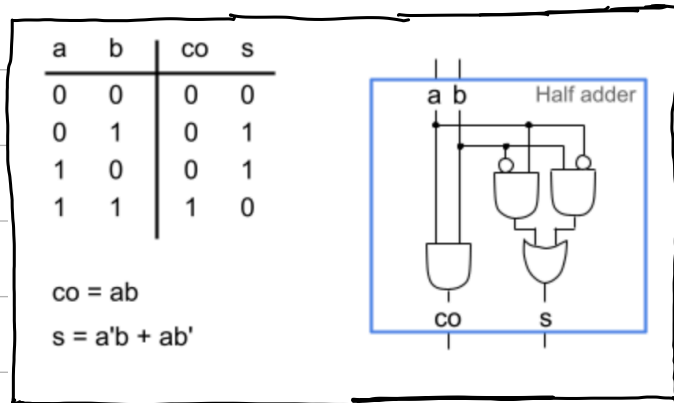↳ half adder truth table equations and circuits:





11.5 Subtractors

• A subtractor computes $A - B$, where A and B are N -bit numbers, such as 8-bit numbers.



↳ If numbers are represented using two's complement representation, a subtractor can be built using an adder.

 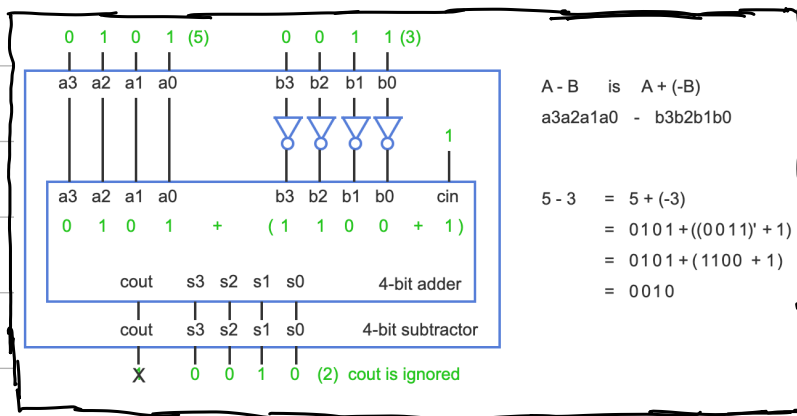↳ Inverting B 's bits and setting the adder's carry-in to 1 add B 's complement to A .



• Because two's complement representation performs subtraction by complementing and adding, a single adder circuit can perform either addition or subtraction, saving circuit size.

• A 4 bit adder/subtractor :

 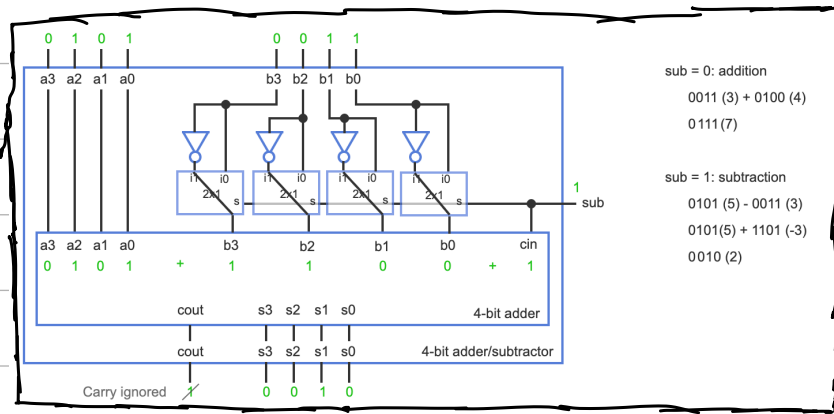

• Configuring the adder/subtractor to perform the following operation: $7 - 2$

$$a_3 a_2 a_1 a_0 = 0111$$

$$b_3 b_2 b_1 b_0 = 0010$$

$$sub = 1$$